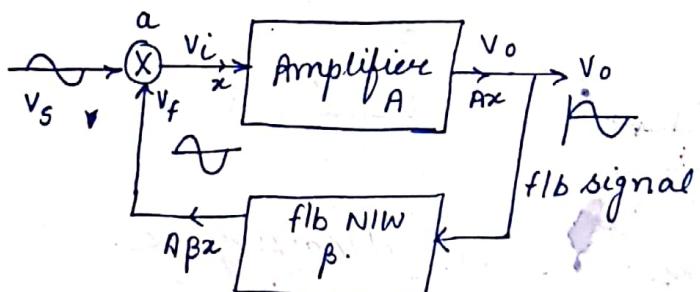


## Sinusoidal Oscillators.

- **Introduction :-** An oscillator is a waveform generator that generates waveform of constant amplitude which oscillates at constant desired freq.
- desired freq. can be obtained by varying ckt parameters.
  - If o/p signal is sinusoidal in nature then sinusoidal osc.
  - able to generate the waveform of very high freq. to low freq. is limited by size of component.
  - gnd & cap. become bulky at lower freq.
  - oscillator uses +ve f/b.
  - osc. does not require any i/p signal.

2. **Basic theory of oscillator :-** It uses positive f/b. as we know that

$$A_f = \frac{A}{1 - A\beta}$$



Now considering various value of  $\beta$  and  $A = 20$ . and Now calculate  $A_f$ .

$A$	$\beta$	$A_f$
20	0.005	22.22
20	0.04	100
20	0.045	200
20	0.05	$\infty$


This result shows that the gain with f/b  $\propto$  as the amount of positive f/b  $\beta$ . Signal  $x$  is applied to i/p whose gain is  $A$ , so o/p is  $xA$ . o/p is passed through f/b NIW whose gain is  $\beta$ . o/p is connected to pt. a and source is removed. Now new i/p is  $ABx$  and o/p is

available without any source. Source is required only once to start process. ~~GE~~

It must be noted that  $\beta < 1$ ; otherwise  $A_f = -ve$ . To start oscillations  $AB > 1$  but the ckt adjust itself to get  $AB = 1$ . it produces sinusoidal osc.

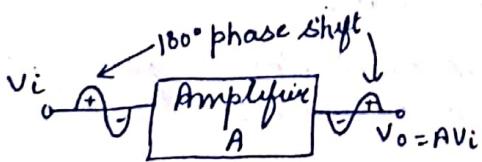3. **Barkhausen criterion :** As Basic Amplifier is inverting, it produces a phase shift of  $180^\circ$  b/w i/p & o/p. But the

f/b must be positive and  $V_o$  is in phase with  $V_i$ . Thus f/b NIW must introduce a phase shift of  $180^\circ$ . This ensures +ve f/b.



$$\therefore V_o = AV_i$$

$$V_f = \beta V_o$$

$$V_f = ABV_i$$

for oscillator, we ~~want~~ want that  $f_{lb}$  should drive the amp. and  $V_f$  must act as a  $V_i$ . hence from above eq<sup>n</sup>

$$|AB\beta| = 1$$

And phase of  $V_f$  is same as  $V_i$ , so  $f_{lb}$  now should introduce  $180^\circ$  phase shift in addition to  $180^\circ$  phase shift introduced by inv. amp.  
So Total phase shift =  $360^\circ$ .

These two condition are known as Barkhausen Criterion.


The B.H. criterion states that :

- (i) The total phase shift  $0 \rightarrow 360^\circ$
- (ii)  $|AB\beta| = 1$ .

Satisfying these condition, the ckt. work as an oscillator.


In reality no i/p signal is needed to start oscillation. Only  $A\beta$  is made greater than 1 to start oscillations. and then ckt. start itself to get  $AB=1$ .

(i)  $|AB\beta| > 1$

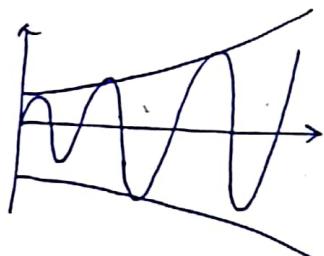


growing type of osc.

(ii)  $|AB\beta| = 1$

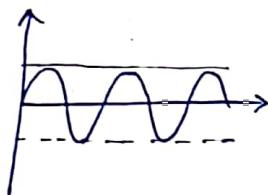

sustained osc.

(iii)

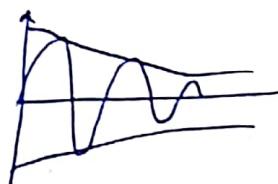

decaying osc.

Starting voltage  $\rightarrow$  Every resistance have some free e-. Under normal room temp. these free e- move randomly in various dir. Such movement of free e- is called generate a vtg. called noise vtg. Such noise vtg. present across the resistance are amplified. Hence to amplify such small noise vtg. and to start oscillation  $|AB\beta| > 1$ .

#### 4. Classification of oscillators : (AB)

(i) based on output waveform / Nature of waveform:

$\rightarrow$  sinusoidal oscillator :- generate sine wave.

$\rightarrow$  Relaxation oscillator / non sinusoidal oscillator :- generate triangular, square, sawtooth waveform.

(ii) based on ckt. component :-

$\rightarrow$  RC oscillator

$\rightarrow$  LC oscillator

$\rightarrow$  crystal oscillator.

(2)

(iii) based on Range of frequency:

- AF : 20 Hz to 200 kHz. (low freq.)
- RF : 20 kHz to 30 MHz.
- HF : 1.5 MHz to 30 MHz
- VHF : 30 MHz to 300 MHz
- UHF : 300 MHz to 3 GHz.
- Microwave : > 3 GHz.

(iv) Whether f<sub>lb</sub> is used or not?

→ f<sub>lb</sub> oscillators : f<sub>lb</sub> is used.

→ Negative resistance oscillators : in which f<sub>lb</sub> is not used to generate oscillation.

5. elements of transistor oscillator : (R.T)


An oscillator contains following 3 elements :

(i) Oscillatory circuit : ~~or~~ these ckt contain parallel combination of L & C. freq. of operation is given as:

$$f = \frac{1}{2\pi\sqrt{LC}} \text{ Hz.}$$

(ii) Internal Amp<sup>H</sup>(A) : amplifies the signal

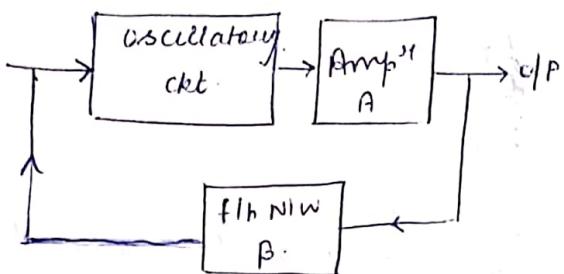(iii) feedback NW : oscillator uses +ve f<sub>lb</sub> NW.



(ii) Transistorised Hartley oscillator : utg divider bias is provided by  $R_1$  &  $R_2$ .  $C_e$  is bypass capacitor &  $C_c$  is coupling capacitor. Tuned ckt is formed by  $L_1, L_2, C$ . Mutual coupling b/w inductor is M and it is positive in nature.  $V_{cc}$  is applied to collector through RFC which permit an easy flow to DC but at same time it offers very high ~~freq~~ imp to high freq. oIP of Tx is coupled back to the Tx iIP through tank ckt. Tx produces phase shift of  $180^\circ$ , another ~~is~~ phase shift of  $180^\circ$  is provided by inductive fb. Thus total phase shift of  $360^\circ$  is obtained.

Working :- As supply is switched on, C is charged through  $V_{cc}$ . This capacitor discharge through  $L_1, L_2$ . oscillation across  $L_1$  are applied to iIP of Tx and appear in amplified form in oIP ckt. This amplified oIP utg. is applied to tuned ckt to feed the losses in tank ckt. oIP is collected across  $L_2$ .

Mathematical Analysis :- (AP)

(4)

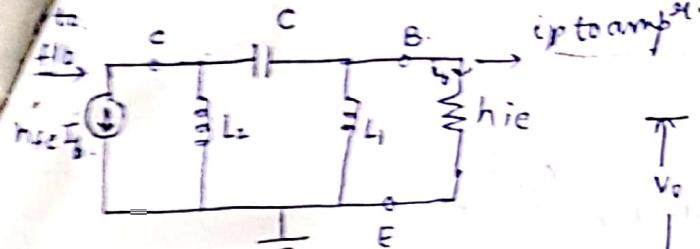


fig: equivalent circ.

Now convert current source to v.tg. source.

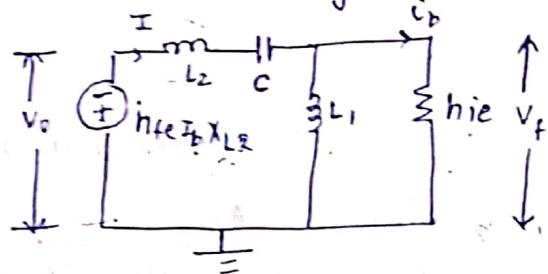


fig: simplified circ.

$$V_o = h_{FE} I_b X_{L2} = h_{FE} I_b j \omega L_2 \quad \text{--- (i)}$$

$$I = \frac{-V_o}{(X_{L2} + X_C) + (X_L || h_{IE})}$$

$$\text{where } X_{L2} + X_C = j \omega L_2 + \frac{1}{j \omega C}$$

$$X_L || h_{IE} = \frac{j \omega L_1 h_{IE}}{j \omega L_1 + h_{IE}}$$

$$I = \frac{-h_{FE} I_b j \omega L_2}{\left( j \omega L_2 + \frac{1}{j \omega C} \right) + \left( \frac{j \omega L_1 h_{IE}}{j \omega L_1 + h_{IE}} \right)} \quad [\text{from eq (i)}]$$

Replace  $j\omega$  by  $s$ .

$$I = \frac{-s h_{FE} I_b L_2}{\left( s L_2 + \frac{1}{s C} \right) + \left( \frac{s L_1 h_{IE}}{s L_1 + h_{IE}} \right)}$$

$$= \frac{-s h_{FE} I_b L_2}{\left( \frac{1 + s^2 L_2 C}{s C} \right) + \left( \frac{s L_1 h_{IE}}{s L_1 + h_{IE}} \right)}$$

$$= \frac{-s h_{FE} I_b L_2 (s C)(s L_1 + h_{IE})}{(1 + s^2 L_2 C)(s L_1 + h_{IE}) + (s C)(s L_1 h_{IE})}$$

$$= \frac{-s^2 c h_{FE} I_b L_2 (s L_1 + h_{IE})}{s L_1 + h_{IE} + s^3 L_2 C + s^2 L_2 C h_{IE} + s^2 C L_1 h_{IE}}$$

$$= \frac{-s^2 h_{FE} I_b L_2 C (s L_1 + h_{IE})}{s^3 L_1 L_2 C + s^2 (L_2 C h_{IE} + C L_1 h_{IE}) + s L_1 + h_{IE}}$$

according to current division rule:

$$I_b = I \frac{X_{L1}}{X_{L1} + h_{IE}} \Rightarrow I_b = \frac{j \omega L_1 \cdot I}{j \omega L_1 + h_{IE}}$$

$$T_0 = \frac{1}{2\pi} \left[ \frac{s_4}{s_4 + h_{ie}} \right]$$

$$T_0 = \frac{-s^3 h_{fe} L_1 L_2 C (s_4 + h_{ie})}{s^3 L_1 L_2 C + s^2 C h_{ie} (L_1 + L_2) + s_4 + h_{ie}} \times \frac{s_4}{(s_4 + h_{ie})}$$

$$T_0 = \frac{-s^2 h_{fe} J_3 L_1 L_2 C}{s^3 L_1 L_2 C + s^2 C h_{ie} (L_1 + L_2) + s_4 + h_{ie}}$$

$$J = \frac{-s^3 h_{fe} L_1 L_2 C}{s^3 L_1 L_2 C + s^2 C h_{ie} (L_1 + L_2) + s_4 + h_{ie}}$$

$$\therefore s = j\omega, s^2 = -\omega^2, s^3 = -j\omega^3$$

$$J = \frac{j\omega^3 h_{fe} L_1 L_2 C}{-j\omega^3 L_1 L_2 C + -\omega^2 C h_{ie} (L_1 + L_2) + j\omega L_1 + h_{ie}}$$

$$J = \frac{j\omega^3 h_{fe} L_1 L_2 C}{[h_{ie} - \omega^2 C h_{ie} (L_1 + L_2)] + j\omega L_1 (1 - \omega^2 L_2 C)}$$

Rationalising the RHS of above eqn

$$J = \frac{j\omega^3 h_{fe} L_1 L_2 C [h_{ie} - \omega^2 C h_{ie} (L_1 + L_2)] - j\omega L_1 (1 - \omega^2 L_2 C)}{[h_{ie} - \omega^2 C h_{ie} (L_1 + L_2)]^2 + \omega^2 L_1^2 (1 - \omega^2 L_2 C)^2}$$

To satisfy this eqn, it becomes necessary that

$$J = \frac{\omega^4 h_{fe} L_1^2 L_2 C (1 - \omega^2 L_2 C) + j\omega^3 h_{fe} L_1 L_2 C [h_{ie} - \omega^2 C h_{ie} (L_1 + L_2)]}{[h_{ie} - \omega^2 C h_{ie} (L_1 + L_2)]^2 + \omega^2 L_1^2 (1 - \omega^2 L_2 C)^2}$$

To satisfy this eqn,  
imaginary part  
must be zero

$$\omega^3 h_{fe} L_1 L_2 C [h_{ie} - \omega^2 C h_{ie} (L_1 + L_2)] = 0$$

$$h_{ie} = \omega^2 C h_{ie} (L_1 + L_2)$$

$$J = \omega^2 C (L_1 + L_2)$$

$$\omega^2 = \frac{L}{C(L_1 + L_2)}$$

replace  $(L_1 + L_2)$  by  $L_{eq}$ .

$$\omega^2 = \frac{L}{C L_{eq}}$$

$$\omega = \frac{1}{\sqrt{C L_{eq}}}$$

$$f = \frac{1}{2\pi \sqrt{C L_{eq}}}$$

The above eqn gives the freq. of oscillation and value of  $h_{fe}$  can be calculated, by equating the magnitudes of both sides:

$$L = \frac{w^4 h_{fe} L_1^2 L_2 C (1 - w^2 L_2 C)}{\left[ h_{ie} - w^2 C h_{ie} (L_1 + L_2) \right]^2 + w^2 L_1^2 (1 - w^2 L_2 C)^2} \quad \text{at } w = \frac{1}{\sqrt{C(L_1 + L_2)}} \quad (5)$$

$$L = \frac{w^4 h_{fe} L_1^2 L_2 C (1 - w^2 L_2 C)}{\left[ h_{ie} - \frac{C h_{ie} (L_1 + L_2)}{C(L_1 + L_2)} \right]^2 + w^2 L_1^2 (1 - w^2 L_2 C)^2}$$

$$L = \frac{w^4 h_{fe} L_1^2 L_2 C (1 - w^2 L_2 C)}{w^2 L_1^2 (1 - w^2 L_2 C)^2}$$

$$L = \frac{w^2 h_{fe} L_2 C}{(1 - w^2 L_2 C)}$$


$$L = \frac{h_{fe} L_2 C}{C(L_1 + L_2)} \Rightarrow L = \frac{h_{fe} L_2 C}{CL_1 + CL_2 - CL_2}$$

$$\left[ 1 - \frac{L_2 C}{C(L_1 + L_2)} \right]$$

$$L = \frac{h_{fe} CL_2}{CL_1}$$

$$L = \frac{h_{fe} L_2}{L_1}$$
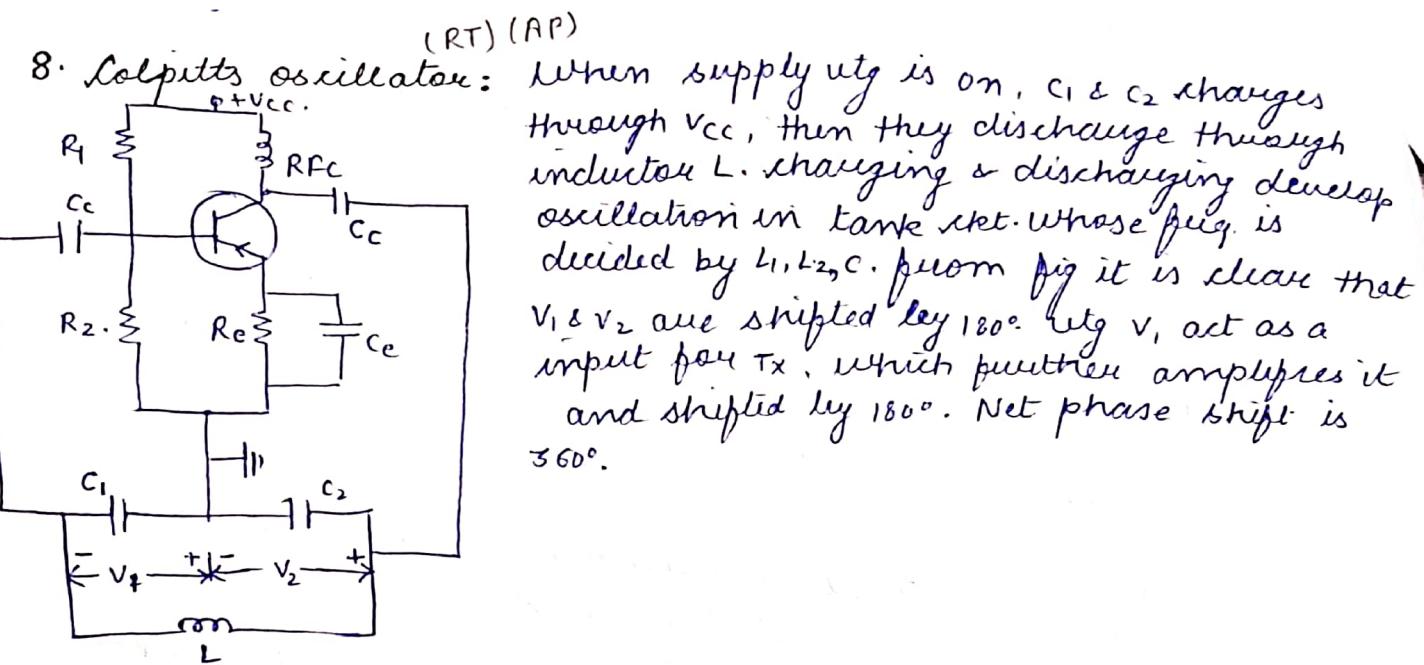
$$h_{fe} = \frac{L_1}{L_2}$$
 This is the value of  $h_{fe}$  required to satisfy the oscillating condition.



When supply voltage is on,  $C_1$  &  $C_2$  charges through  $V_{CC}$ , then they discharge through inductor  $L$ . charging & discharging develop oscillation in tank circ. whose freq. is decided by  $L_1, L_2, C$ . From fig it is clear that  $V_1$  &  $V_2$  are shifted by  $180^\circ$ .  $V_1$  act as a input for  $T_x$ , which further amplifies it and shifted by  $180^\circ$ . Net phase shift is  $360^\circ$ .

### Mathematical Analysis :

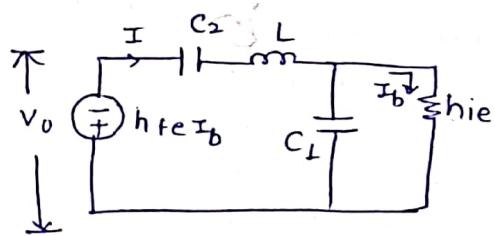
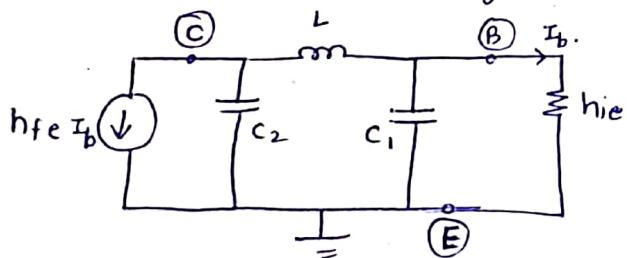


fig: equivalent circuit

$$V_o = hfe I_b \times C_2 = hfe I_b \frac{1}{j\omega C_2}$$

$$I = \frac{-V_o}{(X_{C_2} + X_L) + (X_C || hie)}$$

where,  $X_{C_2} + X_L = \frac{1}{j\omega C_2} + j\omega L$

$$X_C || hie = \frac{hie}{j\omega C_1} \parallel \frac{1}{j\omega C_1}$$

$$I = \frac{-h_{FE} I_b}{j\omega C_2} \cdot \frac{1}{\left[ \frac{1}{j\omega C_2} + j\omega L \right] + \left[ \frac{\frac{h_{IE}}{j\omega C_1}}{h_{IE} + \frac{1}{j\omega C_1}} \right]}$$

replace  $j\omega$  by  $s$ .

$$I = \frac{-h_{FE} I_b}{sC_2} \Rightarrow I = \frac{-h_{FE} I_b}{\left( \frac{1}{sC_2} + sL \right) + \left[ \frac{\frac{h_{IE}}{sC_1}}{h_{IE} + \frac{1}{sC_1}} \right]} \quad \left( \frac{1+s^2LC_2}{sC_2} \right) + \left[ \frac{h_{IE}}{h_{IE}sC_1 + 1} \right]$$

$$I = \frac{-h_{FE} I_b (sC_2)(h_{IE}sC_1 + 1)}{(sC_2) \left[ (1+s^2LC_2)(1+h_{IE}sC_1) + (h_{IE})(sC_2) \right]}$$

$$I = \frac{-h_{FE} I_b (1 + sC_1 h_{IE})}{(s^3LC_1C_2h_{IE} + s^2LC_2 + sh_{IE}(C_1 + C_2) + 1)}$$

$$I = \frac{-h_{FE} I_b (1 + sC_1 h_{IE})}{s^3LC_1C_2h_{IE} + s^2LC_2 + sh_{IE}(C_1 + C_2) + 1}$$

according to current division rule:

$$I_b = I \times \frac{x_{C_1}}{(x_{C_1} + h_{IE})} \Rightarrow I_b = \frac{I}{j\omega C_1} \cdot \frac{1}{h_{IE} + \frac{1}{j\omega C_1}}$$

$$I_b = \frac{I}{1 + sh_{IE}C_1}$$

$$I_b = \frac{-h_{FE} I_b}{s^3LC_1C_2h_{IE} + s^2LC_2 + sh_{IE}(C_1 + C_2) + 1}$$

$$I = \frac{-h_{FE}}{s^3LC_1C_2h_{IE} + s^2LC_2 + sh_{IE}(C_1 + C_2) + 1}$$

replace  $s = j\omega$ ,  $s^2 = -\omega^2$ ,  $s^3 = -j\omega^3$

$$I = \frac{-h_{FE}}{-j\omega^3LC_1C_2h_{IE} - \omega^2LC_2 + j\omega h_{IE}(C_1 + C_2) + 1}$$

$$I = \frac{-h_{FE}}{(1 - \omega^2LC_2) + j\omega h_{IE}[C_1 + C_2 - \omega^2LC_1C_2]} \quad -(i)$$

To satisfy the eqn' imaginary part must be zero.

while  $[C_1 + C_2 - N^2 L C_1 C_2] = 0$

$$\omega^2 = \frac{C_1 + C_2}{L C_1 C_2}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\omega^2 = \frac{1}{L C_{eq}}$$

$$\omega = \frac{1}{\sqrt{L C_{eq}}}$$

$$\boxed{\omega_f = \frac{1}{2\pi\sqrt{L C_{eq}}}}$$

Substitute the value of  $\omega$  in eqn (i)

$$1 = \frac{-hfe}{\left[ 1 - \frac{(C_1 + C_2)L C_2}{L C_1 C_2} \right] + \text{fwhile} \left[ C_1 + C_2 - \frac{L C_1 C_2}{L C_1 C_2} (C_1 + C_2) \right]}$$

$$1 = \frac{-hfe}{\frac{C_1 + C_2 - L (C_1 + C_2)}{C_1} + 0}$$

$$1 = \frac{-hfe}{-C_2/C_1}$$


$$\boxed{\frac{C_1}{C_2} = hfe}$$

g. RC phase shift oscillator : (RT) (AP)

We have studied L-C oscillators, which generate high freq. oscillation. These can not be used for generating low freq. oscillation. (17)

As we know  $f \propto \frac{1}{\sqrt{L}}$  therefore generating low freq. signal requires high value of  $L$ , means it requires bulky inductor, which is expensive and det. miniaturization will not be possible. for generating audio freq. signals RC phase shift & twin T bridge osc. are used.

principle of operation :

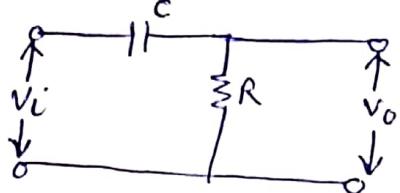

$$\frac{V_o}{V_i} = \frac{R}{R + \frac{1}{j\omega C}} \Rightarrow \frac{V_o}{V_i} = \frac{j\omega CR}{1 + j\omega CR}$$

$$\frac{V_o}{V_i} = \frac{\omega CR \angle 90^\circ}{\sqrt{1 + \omega^2 C^2 R^2} / \tan^{-1} \omega CR}$$

$$\frac{V_o}{V_i} = \frac{\omega CR}{\sqrt{1 + \omega^2 C^2 R^2}} \angle 90^\circ - \tan^{-1} \omega CR.$$

from above expression it is clear that  $V_{tg}$  across  $R$  leads  $V_i$  by an angle  $\phi = 90^\circ - \tan^{-1} \omega CR$ .

But practically  $R$  &  $C$  are so selected that  $\phi$  is nearly equal to  $60^\circ$ .

Total phase shift required is  $180^\circ$ . To obtain these three section of  $90^\circ$  each are required.

OIP of Tx is connected at iip end while OIP of phase shift N/W is connected at iop of Tx.

Tx provides phase shift of  $180^\circ$  & phase shift N/W provide  $180^\circ$ . ~~It is also from eqn. that~~

advantages :

- provide good freq. stability.
- it can be used for producing oscillation of low freq.
- it does not require inductor or transformer.

disadvantages :

- can be used at high freq.
- f<sub>t</sub> is small, not easy to start oscillation
- OIP of osc is comparatively small.

(ii) Transistorised phase shift oscillator :

practical transistorised RC phase shift oscillator consist of single stage amplifier and phase shifting N/W consist of three identical RC section.

Mathematical Analysis :

$h_{ie}$  = i/p imp of amp stage

$R_3$  &  $h_{ie}$  is in series

$$R = R_3 + h_{ie}$$

if  $R_1$  &  $R_2$  are considered then

$$R' = R_1 \parallel R_2 \parallel h_{ie}$$

value of  $R_3$  must be

$$R' + R_3 = R$$

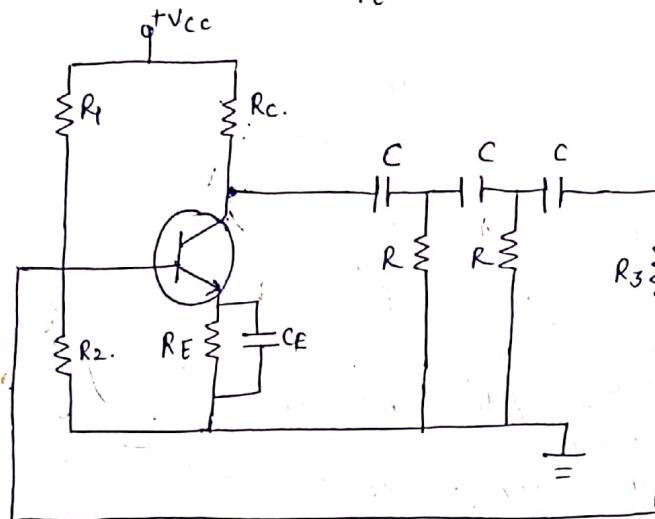


fig: Phase shift osc. using Tx.

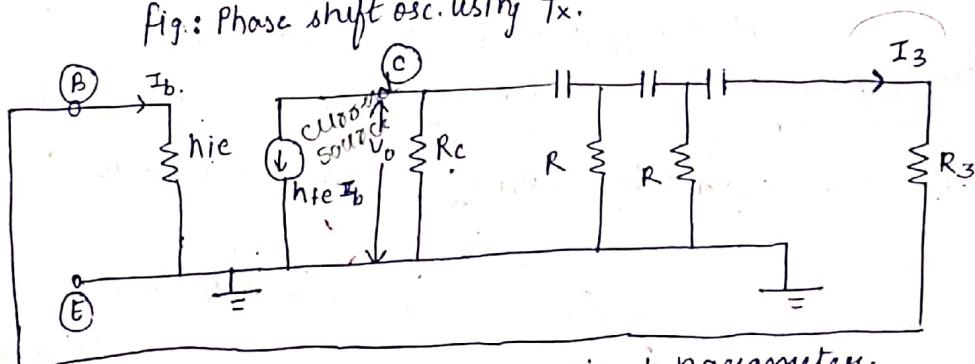


fig: equivalent ckt. using h parameter.

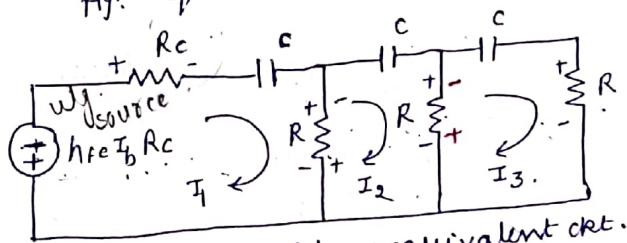


fig: Modified equivalent ckt.

Assume the Ratio of  $R_c$  to  $R$  be  $K$ .

$$K = \frac{R_c}{R}$$

for loop 1 :

$$-I_1 R_c - \frac{I_1}{j\omega C} - I_2 R + I_2 R - h_{fe} I_b R_c = 0$$

Replace  $R_c$  by  $KR$  and  $j\omega = s$ .

$$I_1 \left[ \frac{1}{sC} + (1+K)R \right] - I_2 R = -h_{fe} I_b K R.$$

$$\text{i/p of } f_{lb} = \text{o/p of } \\ \text{Amp} = h_{fe} I_b$$

$$\text{i/p of Amp } i_{lb} = i_p \\ \text{o/p of } f_{lb} = i_3$$

$$\beta = \frac{i_3}{h_{fe} I_b}$$

$$A = \frac{h_{fe} I_b}{I_b}$$

$$AB = \frac{i_3}{I_b}$$

for loop 2:

$$-\frac{1}{jwc} I_2 - I_2 R - I_2 R + I_1 R + I_3 R = 0$$

$$-I_1 R + I_2 \left[ 2R + \frac{1}{sc} \right] - I_3 R = 0$$

for loop 3:

$$-\frac{I_3}{jwc} - I_3 R - I_3 R + I_2 R = 0$$

$$-I_2 R + I_3 \left[ 2R + \frac{1}{sc} \right] = 0$$

Using Crammer's Rule to solve for  $I_3$ :

$$D = \begin{vmatrix} (k+1)R + \frac{1}{sc} & -R & 0 \\ -R & 2R + \frac{1}{sc} & -R \\ 0 & -R & 2R + \frac{1}{sc} \end{vmatrix}$$

$$D = \left[ (k+1)R + \frac{1}{sc} \right] \left[ \left( 2R + \frac{1}{sc} \right)^2 - R^2 \right] + R \left[ (-R)(2R + \frac{1}{sc}) \right]$$

$$D = \left[ (k+1)R + \frac{1}{sc} \right] \left( 2R + \frac{1}{sc} \right)^2 - R^2 \left[ (k+1)R + \frac{1}{sc} \right] - R^2 \left( 2R + \frac{1}{sc} \right)$$

$$D = \frac{SCR(k+1)+1}{S^3C^3} [2RSC+1]^2 - \frac{R^2[2RSC+1]}{SC} - \frac{R^2[(k+1)SCR+1]}{SC}$$

~~first term can be written as~~

$$D = \frac{[KSCR+SCR+1][4R^2S^2C^2+L+4RSC]}{S^3C^3} + \frac{-R^2[2RSC+1+L+KSCR+SCR]}{SC}$$

$$D = \frac{4KS^3R^3C^3 + KSCR + 4KS^2C^2R^2 + 4S^3R^3C^3 + SCR + 4R^2S^2C^2 + 4R^2S^2C^2 + L}{S^3C^3} + \frac{4R^2S^2C^2 + L}{4RCRS}$$

$$-R^2[2RSC+2+KSCR+SCR]$$

$$D = \frac{4KS^3R^3C^3 + 4S^3R^3C^3 + 4KS^2R^2C^2 + 8R^2S^2C^2 + (5+K)SCR - \frac{L}{3SCR}}{S^3C^3} - 2R^2 \frac{\cancel{S^3C^3}}{\cancel{S^2C^2}} - 2R^2 \frac{3^3}{\cancel{S^2C^2}} \cancel{R} \cancel{SCR}^3$$

$$D = \frac{3KS^3R^3C^3 + 4KS^2R^2C^2 + (S^3R^3C^3 + (5+K)SCR + 6R^2S^2C^2 + L)}{S^3C^3}$$

$$D = \frac{S^3R^3C^3[3K+1] + S^2R^2C^2[4K+6] + SRC[5+K] + L}{S^3C^3}$$

$$D_3 = \begin{vmatrix} (K+1)R + \frac{1}{SC} & -R & -h_{fe} I_b K R \\ -R & 2R + \frac{1}{SC} & 0 \\ 0 & -R & 0 \end{vmatrix}$$

$$D_3 = -R^2 (h_{fe} I_b K R)$$

$$= -K R^3 h_{fe} I_b$$

$$I_3 = \frac{D_3}{D}$$

$$I_3 = \frac{-K R^3 h_{fe} I_b S^3 C^3}{S^3 R^3 C^3 (3K+1) + S^2 C^2 R^2 (4K+6) + S C R (5+K) + 1}$$

$I_b$  = i<sub>IP</sub> current to amp.

$I_c$  = i<sub>IP</sub> current to f/b ckt.;  $I_c = h_{fe} I_b$ .

$I_3$  = o<sub>IP</sub> current of f/b ckt.;

$$\beta = \frac{\text{oIP of f/b ckt.}}{\text{iIP of f/b ckt.}} = \frac{I_3}{h_{fe} I_b}$$

$$A = \frac{\text{oIP of Amp ckt.}}{\text{iIP of Amp ckt.}} = \frac{h_{fe} I_b}{I_3} = h_{fe}$$

$$A\beta = \frac{I_3}{h_{fe} I_b} \times h_{fe} \Rightarrow A\beta = \frac{I_3}{I_b}$$

$$A\beta = \frac{-K R^3 h_{fe} S^3 C^3}{S^3 R^3 C^3 (3K+1) + S^2 C^2 R^2 (4K+6) + S C R (5+K) + 1}$$

Replace  $S = j\omega$ ,  $S^2 = -\omega^2$ ,  $S^3 = -j\omega^3$

$$A\beta = \frac{j\omega^3 K R^3 C^3 h_{fe}}{-j\omega^3 R^3 C^3 (3K+1) - \omega^2 C^2 R^2 (4K+6) + j\omega C R (5+K) + 1}$$

$$A\beta = \frac{j\omega^3 K R^3 C^3 h_{fe}}{\left[1 - 4K\omega^2 R^2 C^2 - 6\omega^2 R^2 C^2\right] - j\omega [3K\omega^2 R^3 C^3 + \omega^2 R^3 C^3 + 5CR - KCR]}$$

Dividing Num & Den. by  $(-j\omega^3 R^3 C^3)$

$$A\beta = \frac{-K h_{fe}}{\left\{ \frac{1 - 4K\omega^2 R^2 C^2 - 6\omega^2 R^2 C^2}{-j\omega^3 R^3 C^3} \right\} - j\omega \left\{ \frac{3K\omega^2 R^3 C^3 + \omega^2 R^3 C^3 - 5CR - KCR}{-j\omega^3 R^3 C^3} \right\}}$$

Replace  $-1/j = j$ .

$$A\beta = j \left\{ \frac{1}{W^3 R^3 C^3} - \frac{4K}{W R C} - \frac{6}{W R C} \right\} + \left\{ \frac{3K + L - 5}{W^2 R^2 C^2} - \frac{K}{W^2 R^2 C^2} \right\}$$

replace  $\frac{1}{WRC} = \alpha$

(9)

$$AB = -Khf_e \quad \text{--- (i)}$$

$$\{3k+1-5\alpha^2-k\alpha^2\} + j\{\alpha^3-4k\alpha-6\alpha\}$$

~~As per Barkhausen criterion  $\angle AB = 0^\circ$ . Now the angle of Numer term  $-Khf_e$  is  $0^\circ$ . Hence to have angle of the num term as  $0^\circ$ , imaginary part of Num must be  $0^\circ$ .~~

To have phase shift of  $180^\circ$ , imaginary part must be zero.

$$\alpha^3 - 4k\alpha - 6\alpha = 0$$

$$\alpha(\alpha^2 - 4k - 6) = 0$$

$$\alpha^2 = 4k + 6$$

$$\frac{1}{WRC} = \sqrt{4k+6}$$

$$W = \frac{L}{R C \sqrt{4k+6}}$$

$$f = \frac{1}{2\pi R C \sqrt{4k+6}}$$

$$\tan^{-1}\left(\frac{\alpha}{\omega}\right) = \tan^{-1}(0)$$

$$180^\circ = \tan^{-1}(1)$$

This is the freq. at which  $\angle AB = 0^\circ$  and  $|AB| = 1$

Substitute  $\alpha = \sqrt{4k+6}$  in eqn (i)

$$AB = -Khf_e$$

$$\{3k+1 - 5(4k+6) - k(4k+6)\} + j\{(4k+6)^{3/2} - 4k\sqrt{4k+6} - 6\sqrt{4k+6}\}$$

$$AB = \frac{-Khf_e}{\{3k+1 - 20k - 30 - 4k^2 - 6k\} + j\sqrt{4k+6}\{4k+6 - 4k - 6\}}$$

$$AB = \frac{-Khf_e}{-3k - 29 - 20k - 4k^2}$$

$$AB = \frac{-Khf_e}{-4k^2 - 23k - 29}$$

NOW.  $|AB| = 1$

$$\left| \frac{-Khf_e}{-4k^2 - 23k - 29} \right| = 1$$

$$Khf_e = 4k^2 + 23k + 29$$

$$hfe = \frac{4k^2 + 23k + 29}{k} \quad \text{--- (ii)}$$

Minimum value of  $hfe$ :

$$\text{To get min value; } \frac{dhfe}{dk} = 0$$

$$\frac{-Khf_e \{ (3k+1-5\alpha^2-k\alpha^2) + jKhf_e (\alpha^3-4k\alpha-6\alpha) \}}{(3k+1-5\alpha^2-k\alpha^2)^2 + (\alpha^3-4k\alpha-6\alpha)^2}$$

$$\frac{-Khf_e (3k+1-5\alpha^2-k\alpha^2)}{(3k+1-5\alpha^2-k\alpha^2)^2 + (\alpha^3-4k\alpha-6\alpha)^2}$$

$$3k+1 - 5(4k+6) - k(4k+6) \\ 3k+1 - 20k - 30 - \frac{4k^2 - 6}{k} \\ -4k^2 - 33k - 29 = 0$$

$$\frac{d}{dk} \left[ 4k + 23 + \frac{29}{k} \right] = 0$$

$$\cancel{4k} - \frac{4 - 29}{k^2} = 0$$

$$k^2 = \frac{29}{4}$$

$$k = 2.6925 \text{ for min. hfc.}$$

Substitute these values in eqn (ii)

$$(hfe)_{min} = 44.54$$

Thus for the ckt to oscillate, we must select the  $T_x$  whose  $(hfe)_{min}$  should be greater than 44.54.

# 10. Wein bridge oscillator : (AP)

(11)

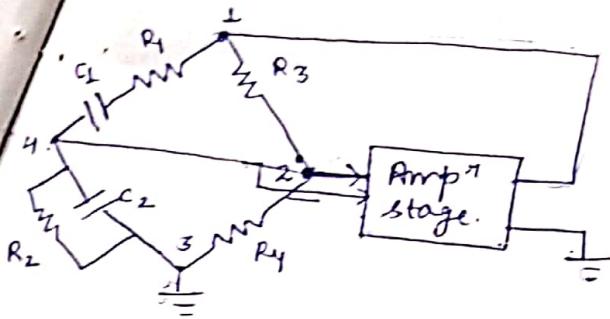


Fig 1: Basic ckt.

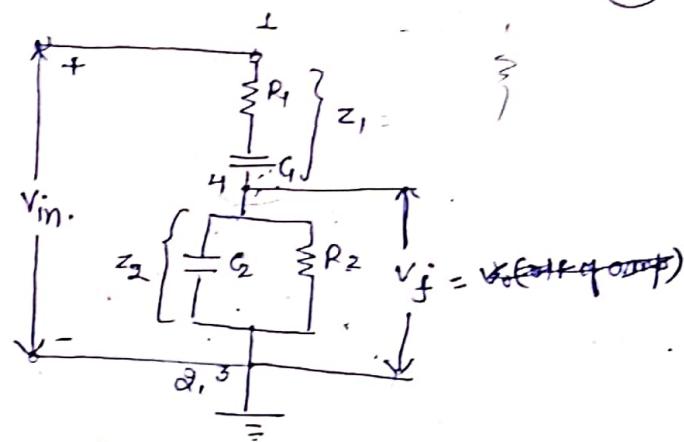


Fig 2: f/b Network.

Generally in oscillators amplifier introduces  $180^\circ$  phase shift and HB introduces  $180^\circ$ , to obtain  $360^\circ$  around a loop. This is required condition of any oscillator. But Wein bridge uses non inverting amp and hence doesn't provide any phase shift during amp stage. As total phase shift required is  $0^\circ$  or  $360^\circ$ , in Wein bridge no phase shift is necessary through HB. Thus total phase shift is  $0^\circ$ .

O/P of Amp  $\rightarrow$  1 & 3  $\rightarrow$  I/P of HB NW

I/P of Amp  $\rightarrow$  2 & 4  $\rightarrow$  O/P of HB NW

two arms  $R_1, C_1 \rightarrow$  series freq. sensitive arms. because component   
  $R_2, C_2 \rightarrow$  parallel of these arms decide the freq. of osc.

It is most popular osc. and used for audio freq. range (20 to 20 KHz)

advantages :-

$\rightarrow$  ckt. provide good freq. stability

$\rightarrow$  very good sine wave o/p.

$\rightarrow$  overall gain being a product of gain of 2 stages is very high.

$\rightarrow$  freq. of osc. can be varied in the range of 10 MHz as compared to

RC phase shift osc.

disadvantages :

$\rightarrow$  osc. can not be used at high freq.

$\rightarrow$  2 stage Tx amp is used hence large no. of component required.

Limitation of LC or RC oscillators :-

$\rightarrow$  The major problem with these osc. is that freq. does not remain strictly constant. This is because value of R & C changes with temp. To overcome this problem crystal osc. are used which have excellent freq. stability.

Mathematical Analysis :-


from fig. 2.

$$Z_1 = R_1 + \frac{1}{j\omega C_1} = \frac{1 + j\omega R_1 C_1}{j\omega C_1}$$

$$Z_2 = R_2 \frac{1}{j\omega C_2} = \frac{R_2}{j\omega C_2} = \frac{R_2}{1 + j\omega R_2 C_2}$$

Replace  $S = j\omega$
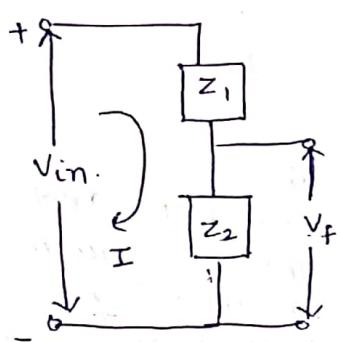
$$Z_1 = \frac{1 + SR_1 C_1}{SC_1}, Z_2 = \frac{R_2}{1 + SR_2 C_2}$$



$$I = \frac{V_{in}}{Z_1 + Z_2}$$

$$V_f = I Z_2$$

$$V_f = \frac{V_{in} Z_2}{Z_1 + Z_2}$$

$$\beta = \frac{V_f}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}$$

Substitute the value of  $Z_1$  &  $Z_2$ :

$$\beta = \frac{\frac{R_2}{1 + SR_2 C_2}}{\frac{1 + SR_1 C_1}{SC_1} + \frac{R_2}{1 + SR_2 C_2}} \Rightarrow \beta = \frac{SR_2 C_1}{R_2 S C_1 + (1 + SR_1 C_1)(1 + SR_2 C_2)}$$

$$\beta = \frac{SQR_2}{S R_2 G + 1 + SR_2 C_2 + SR_1 C_1 + S^2 R_1 G R_2 C_2}$$

$$\beta = \frac{SQR_2}{1 + S(R_2 G + R_2 C_2 + R_1 C_1) + S^2 (R_1 R_2 C_1 C_2)}$$

Replace  $S = j\omega$ ,  $S^2 = -\omega^2$ .

$$\beta = \frac{j\omega C_1 R_2}{(1 - \omega^2 R_1 R_2 G C_2) + j\omega (R_1 C_1 + R_2 C_2 + G R_2)}$$

Rationalising the expression:

$$\beta = \frac{j\omega C_1 R_2 [(1 - \omega^2 R_1 R_2 G C_2) \mp j\omega (R_1 C_1 + R_2 C_2 + G R_2)]}{[(1 - \omega^2 R_1 R_2 G C_2) + j\omega (R_1 C_1 + R_2 C_2 + G R_2)][(1 - \omega^2 R_1 R_2 G C_2) \mp j\omega (R_1 C_1 + R_2 C_2 + G R_2)]}$$

$$\beta = \frac{\omega^2 G R_2 (R_1 C_1 + R_2 C_2 + G R_2) + j\omega C_1 R_2 (1 - \omega^2 R_1 R_2 G C_2)}{(1 - \omega^2 R_1 R_2 G C_2)^2 + \omega^2 (R_1 C_1 + R_2 C_2 + G R_2)^2}$$

To have zero phase shift of f/b N/W, its imaginary part must be zero.

$$\omega^2 G R_2 (1 - \omega^2 R_1 R_2 G C_2) = 0$$

$$\omega^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

Above eqn gives the freq. of osc. and it shows that the component of freq. sensitive arm are the deciding factors.

(12)

if  $R_1 = R_2 = R$ ;  $C_1 = C_2 = C$ .

$$f = \frac{1}{2\pi\sqrt{R^2C^2}}$$

$$f = \frac{1}{2\pi RC}$$

At  $R_1 = R_2 = R$  &  $C_1 = C_2 = C$ , the gain of fib NW becomes.

$$\beta = \frac{\omega^2 RC (3RC) + j\omega RC (1 - \omega^2 R^2 C^2)}{(1 - \omega^2 R^2 C^2) + \omega^2 (3RC)^2}$$

$$\text{put } \omega = \frac{1}{RC}$$

$$\beta = \frac{\frac{3R^2C^2}{R^2C^2} + j\frac{RC}{RC} \left(1 - \frac{R^2C^2}{R^2C^2}\right)}{\left(\frac{1 - R^2C^2}{R^2C^2}\right) + \frac{9R^2C^2}{R^2C^2}}$$

$$\beta = \frac{3}{9} = \frac{1}{3}$$

positive sign of  $\beta$  shows that phase shift of fib NW is  $0^\circ$ .

Now to satisfy the Barkhausen criterion for the sustained oscillation.

$$|A\beta| \geq 1$$

$$|A| \geq \frac{1}{|\beta|}$$

$$|A| \geq 3$$

This is required gain of amp<sup>st</sup> stage.

..... also consist

## 11. Crystal oscillator :- (HF)(PT)(AP)

- The crystals are either naturally occurring or synthetically manufactured, exhibit the piezoelectric effect. e.g. quartz, tourmaline, Rochelle salt.
- piezo electric effect :- It means under the influence of the mechanical pressure, the vtg. get generated across the opposite faces of the crystal.
- If the mechanical force is applied in such a way to force the crystal to vibrate, the a.c. vtg. get generated across it. conversely if the crystal is subjected to a.c. vtg., it vibrates causing mechanical distortion in the crystal
- every crystal has its own resonant freq. according to its shape.
- When Application of force rearrange the charges, therefore one surface is +ve charged and other is -ve charged. It produces electrical potential.
- for use in clk, crystal is suitably cut and mounted b/w two metal plate. The device is equivalent to capacitor with quartz as a dielectric


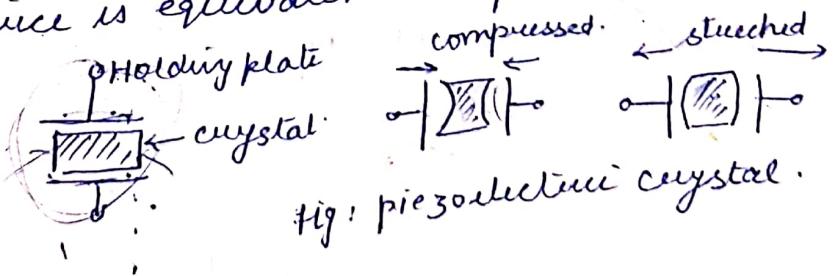


fig: piezoelectric crystal.

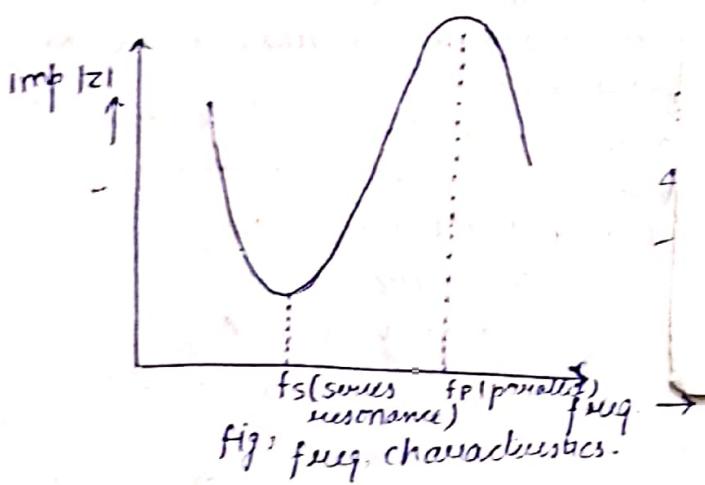

\* Pierce crystal oscillator: Colpitts oscillator can be modified by using crystal to behave as an L.

The colpitts is called pierce crystal osc. two C are required in tank ckt. pierce crystal osc's working is same as colpitts oscillator.

The oscillator ckt can be modified by using internal cap. of Tx. most separate C, L, C2 are not required in such ckt.

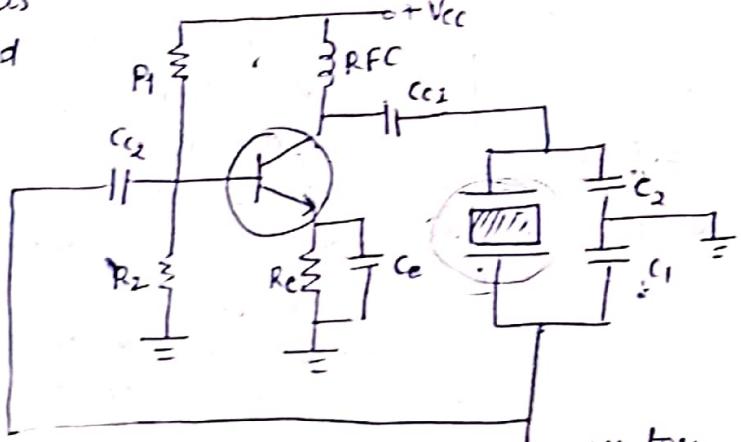


fig: pierce crystal oscillator

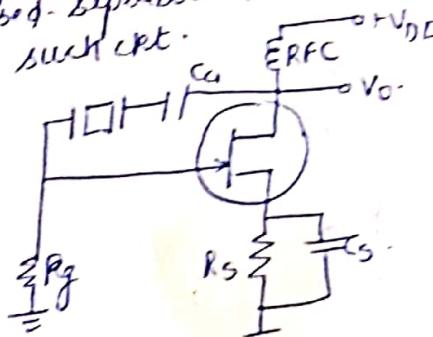


fig: using FET.

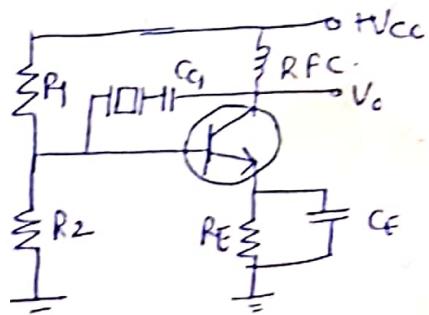


fig: using Tx.

\* Miller crystal oscillator :- Hartley osc. can be modified to get Miller crystal osc. In Hartley osc. two ind. and one cap is required. One L is replace by a crystal. and one L2 C is used.

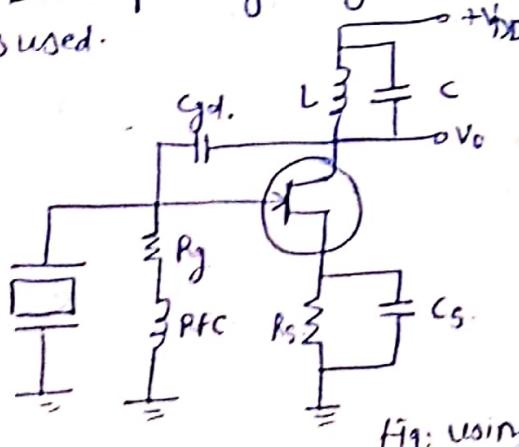


fig: using FET.

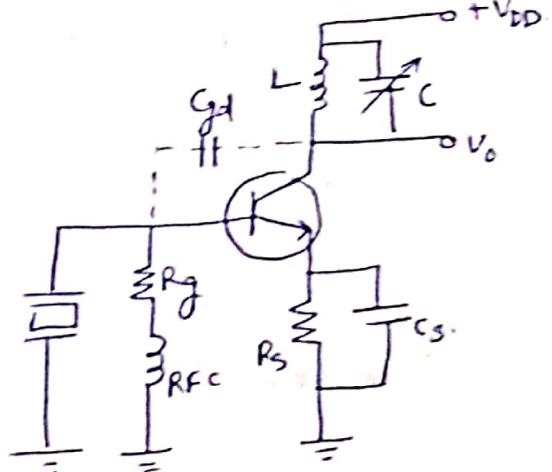


fig: crystal osc

→ crystal oscillator are preferred when greater freq. stability is required. used in watches, & Tx, Rx.

→ main substance is quartz  
→ Rochelle salts have greatest piezoelectric activity. for given a.c. utg, they vibrate more than quartz & tourmaline. but it is mechanically weakest and break very easily.

→ Tourmaline shows least piezoelectric effect but mechanically strongest. very expensive and rarely used.

→ Quartz is compromise b/w them. inexpensive & easily available.  
(\*) electrical equivalent ckt:- when crystal is not vibrating, it is equivalent to mechanical ~~existing~~ mounting of crystal. such a

cap. exist due to two metal plate separated by dielec. slab, called mounting capacitance denoted as  $C_M$ .  
→ when it is vibrating, there are internal frictional losses which is denoted by  $R$ .

→ Mass of crystal is indication of inertia is represented by  $L$ .  
→ In vibrating condition, it is having some stiffness which is represented by  $C$ .

(\*) Series resonance freq. :- (when  $X_L = X_C$ )

$$X_L = X_C$$

$$\omega_{SL} = \frac{1}{\omega_{SC} C}$$

$$\omega_s^2 = \frac{1}{LC}$$

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

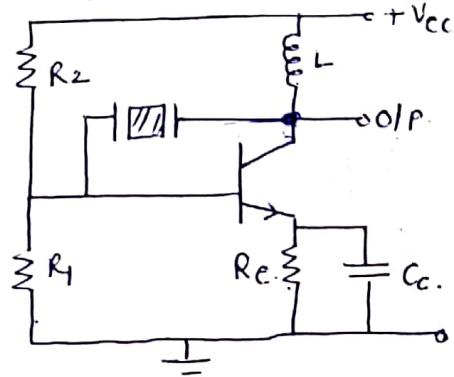


Fig: series resonant mode.

(\*) parallel resonant freq. :-

$$\omega_{PL} = \frac{1}{\omega_{PC}} = \frac{1}{\omega_{PCM}}$$

$$\omega_{PL} = \frac{1}{\omega_{PCM}} + \frac{1}{\omega_{PC}}$$

$$\omega_p^2 = \frac{1}{L(C_M)} + \frac{1}{LC}$$

$$\omega_p^2 = \frac{1}{L} \left[ \frac{C_{CM}}{C + C_M} \right]$$

$$f_p = \frac{1}{2\pi\sqrt{\frac{C_{CM}}{C + C_M}}}$$

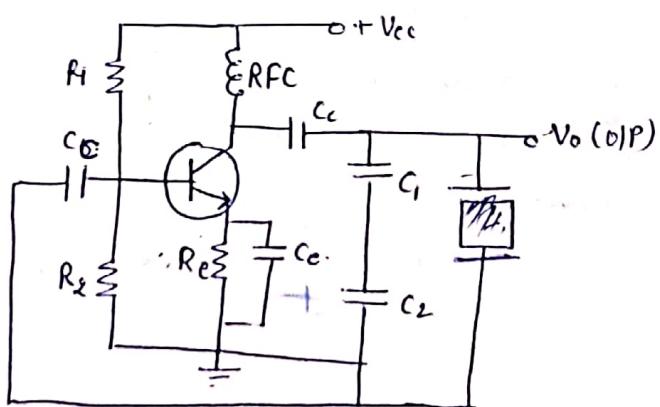


Fig: parallel resonant Mode.